

**Group A**

1. Simplify (Using k-map) the given Boolean function in both SOP and POS using the don't care condition d: and draw a NAND-NAND logic diagram for minimal SOP and NOR-NOR for the minimal POS,  $F(A,B,C,D) = (0,1,3,7,8,12)$  and  $\pi d(5,9,13,14)$ .

2. Design a combinational circuit has four inputs and one output. The output is equal to 1 when (1) all the inputs are equal to 1 or (2) none of the inputs are equal to 1 or (3) an odd number of inputs are equal to 1.

a Obtain the truth table.

b. Find the simplified output function in SOP.

c. Find the simplified output function in POS.

d. Draw the logic diagrams for both SOP and POS.

**Group B**

3. Convert  $(573.35)_8$  into decimal and Hexadecimal.

4. Subtract  $(735.4 - 55.3)$  using both 10's and 9's complement.

5. Perform  $A+B$ ,  $B-A$ :

$A = +19$  and  $B = -37$

6. What is Boolean algebra? Simplify the given Boolean expression using the algebraic method:

$$z(y+z)(x+y+z)$$

7. What is Universal Logic Gate? Realize NAND Gate as Universal Logic Gate.

8 Express the given function in Sum of minterms.

$$F(x, y, z) = x y + z$$

9. Define parity bit? Design 3- bit even parity generator circuit with logic diagram and truth table.

10. Implement full adder circuit using two half adder circuits and one OR gate.